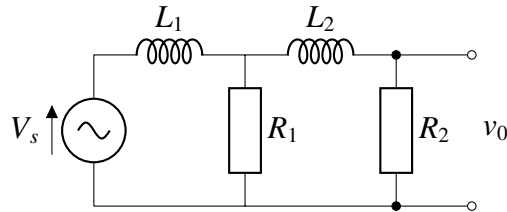


ME 36

EE23BTECH11048-Ponugumati Venkata Chanakya*


QUESTION: In the circuit shown below, $R_1 = 2\Omega$, $R_2 = 1\Omega$, $L_1 = 2$ h, and $L_2 = 0.5$ H. Which of the following describe(s) the correct characteristics of the circuit ?



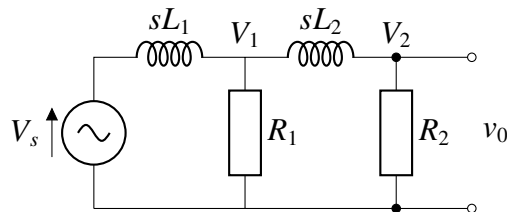- 1) Second order high pass filter
- 2) Second order low pass filter
- 3) Under damped system
- 4) Overdamped system

Solution:

Converting above circuit to frequency domain using laplace transform let V_1 and V_2 be voltages at shown positions



Variable	Value
R_1	2Ω
R_2	1Ω
L_1	2 H
L_2	0.5 H

TABLE 4

INPUT PARAMETERS

$$V_0 = V_1 \left(\frac{R_2}{R_2 + sL_2} \right) \quad (1)$$

$$V_1 = V_s \left(\frac{R_1 \left(\frac{sL_2 + R_2}{R_1 + R_2 + sL_2} \right)}{sL_1 + R_1 \left(\frac{sL_2 + R_2}{R_1 + R_2 + sL_2} \right)} \right) \quad (2)$$

$$V_1 = V_s \left(\frac{2 + s}{(2 + s) + s(6 + s)} \right) \quad (3)$$

$$V_0 = \frac{2}{s^2 + 7s + 2} \quad (4)$$

$$\lim_{s \rightarrow 0} V_0 = V_s(\text{finite}) \quad (5)$$

$$\lim_{s \rightarrow \infty} V_0 = 0 \quad (6)$$

For lower frequency V_0 is finite and for higher frequency V_0 is zero

\therefore Second order low pass filter

From ??

$$s^2 + 7s + 2 = 0 \quad (7)$$

$$\delta = 7^2 - 4(2)(1) \quad (8)$$

$$\delta > 0 \quad (9)$$

\therefore Over-damped System

\therefore B,D are correct options